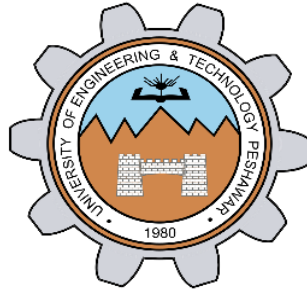


De-Morgan's Theorem

LAB #03



Fall 2025

CSE202L Digital Logic Design Laboratory

Class Section: **A**

Submitted by:

Name: Afaq Aslam

Reg: 24PWCSE2367

Name: Abbas Ali

Reg: 24PWCSE2402

Name: Salman Ahmad

Reg: 24PWCSE2445

Submitted to:

Dr. Rehmat Ullah Khattak

October 10, 2025

Department of Computer Systems Engineering

University of Engineering and Technology, Peshawar

De-Morgan's Theorem:

Objective:

By the end of this experiment, you should be able to:

- Demonstrate De-Morgan's theorems through practical implementation using two input variables.

Required Components:

- 7432 – Quad 2-input OR gate IC
- 7404 – Hex Inverter IC
- LED (Light Emitting Diode)
- 7430 – Quad 2-input AND gate IC
- DIP Switch
- Three resistors (1 kΩ each)


DE-MORGAN'S THEOREM:

- $(X + Y)' = X' \cdot Y'$ (a)
- $(X \cdot Y)' = X' + Y'$ (b)

Procedure:

- Assemble the circuit corresponding to the left-hand side of Equation (a), as illustrated in Figure 3.1. Observe how the LED responds to different input combinations.
- Next, construct the circuit shown in Figure 3.2, representing the right-hand side of Equation (a). Test all possible input combinations using the switches and fill in the truth table (Table 3.1) accordingly.
- Compare the output columns from both circuits to determine if Equation (a) is validated.
- Repeat the same steps for the circuits shown in Figures 3.3 and 3.4 to verify Equation (b) as per De-Morgan's Theorem.

LOGIC CIRCUIT DIAGRAM

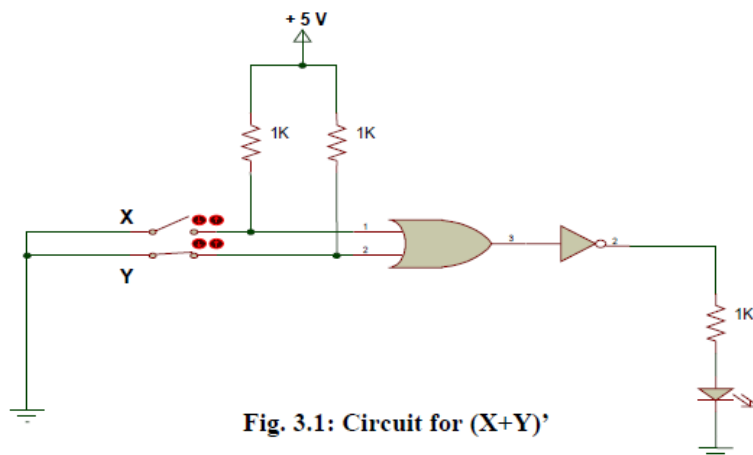


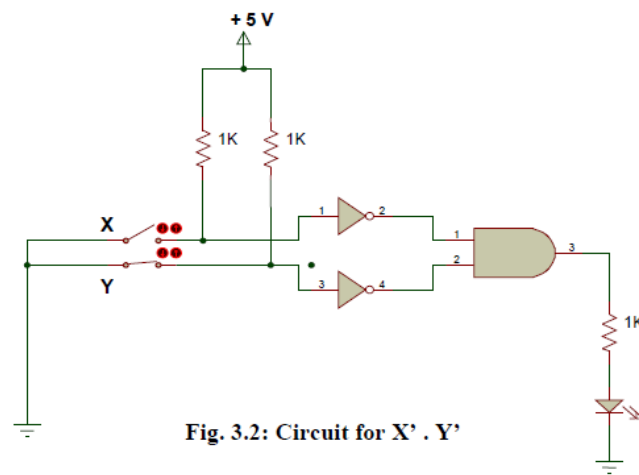
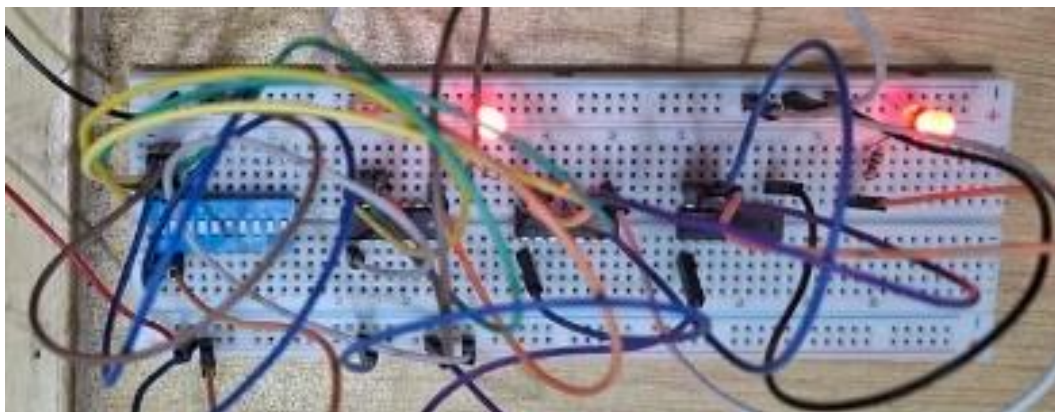


Fig. 3.2: Circuit for $X' \cdot Y'$

Truth Table 3.1:

X	Y	$(X \cdot Y)'$	$(X' + Y')$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Circuit Picture:

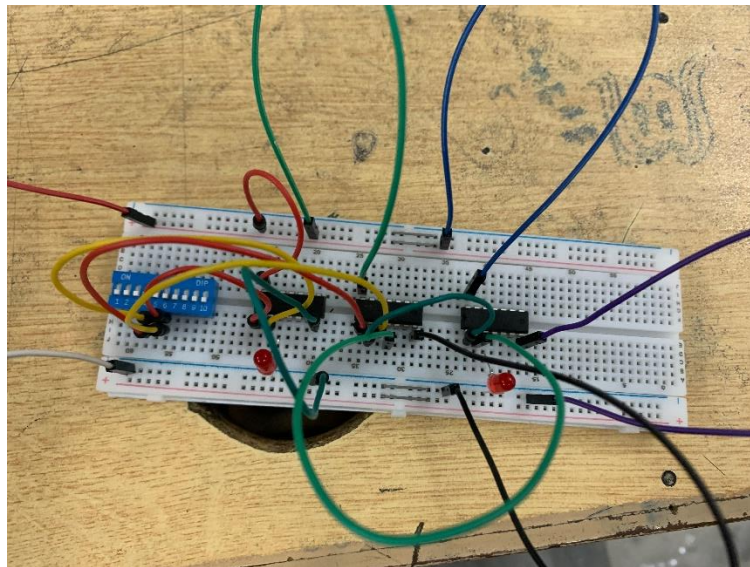

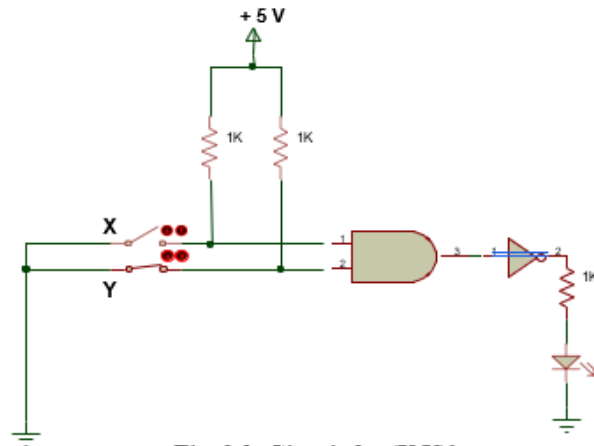


Fig. 3.3: Circuit for $(X.Y)'$

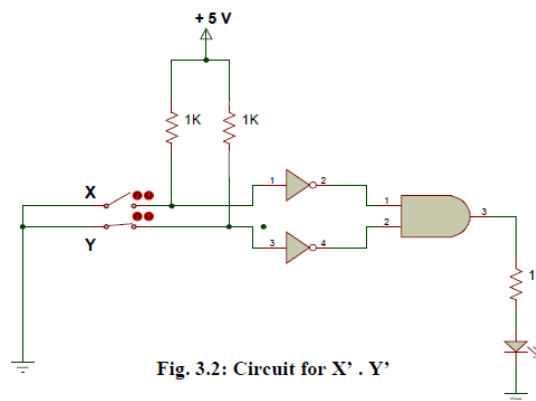


Fig. 3.2: Circuit for $X' . Y'$

Truth Table 3.2:

X	Y	$(X . Y)'$	$(X' + Y')$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

REVIEW QUESTIONS:

- Simplify the expression using De-Morgan's theorems and verify the two expressions experimentally.

$$F = ((A . B)' + A)'$$

ANSWER:


(Task 1)

$$\begin{aligned} F &= ((A \cdot B)' + A)' \\ &= ((A' + B') + A)' \\ &= (\underbrace{A' + A}_{\rightarrow 1} + B')' \\ &= (1 + B')' \\ &= (1)' \\ &= 0 \end{aligned}$$

Truth Table:

A	B	A · B	(A · B)'	(A · B)' + A	((A · B)' + A)'
0	0	0	1	1	0
0	1	0	1	1	0
1	0	0	1	1	0
1	1	1	0	1	0

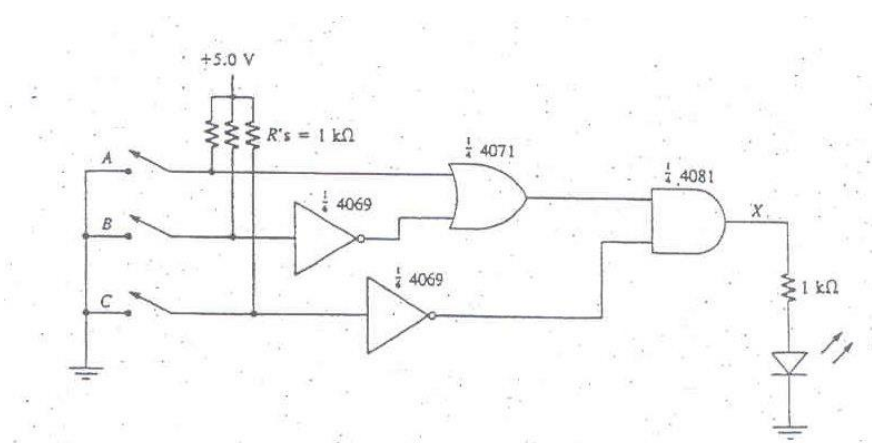- Determine experimentally whether the given circuits are equivalent. Then use De-Morgan's theorem to prove your answer algebraically.





Answer:

$$\begin{aligned} F_1 &= (A+B') \cdot C' \\ &= A \cdot C' + B' \cdot C' \rightarrow \textcircled{a} \end{aligned}$$

$$\begin{aligned} F_2 &= ((A' \cdot B) + C)' \\ &= (A' \cdot B)' \cdot C' \\ &= (A + B') \cdot C' \\ &= A \cdot C' + B' \cdot C' \rightarrow \textcircled{b} \end{aligned}$$

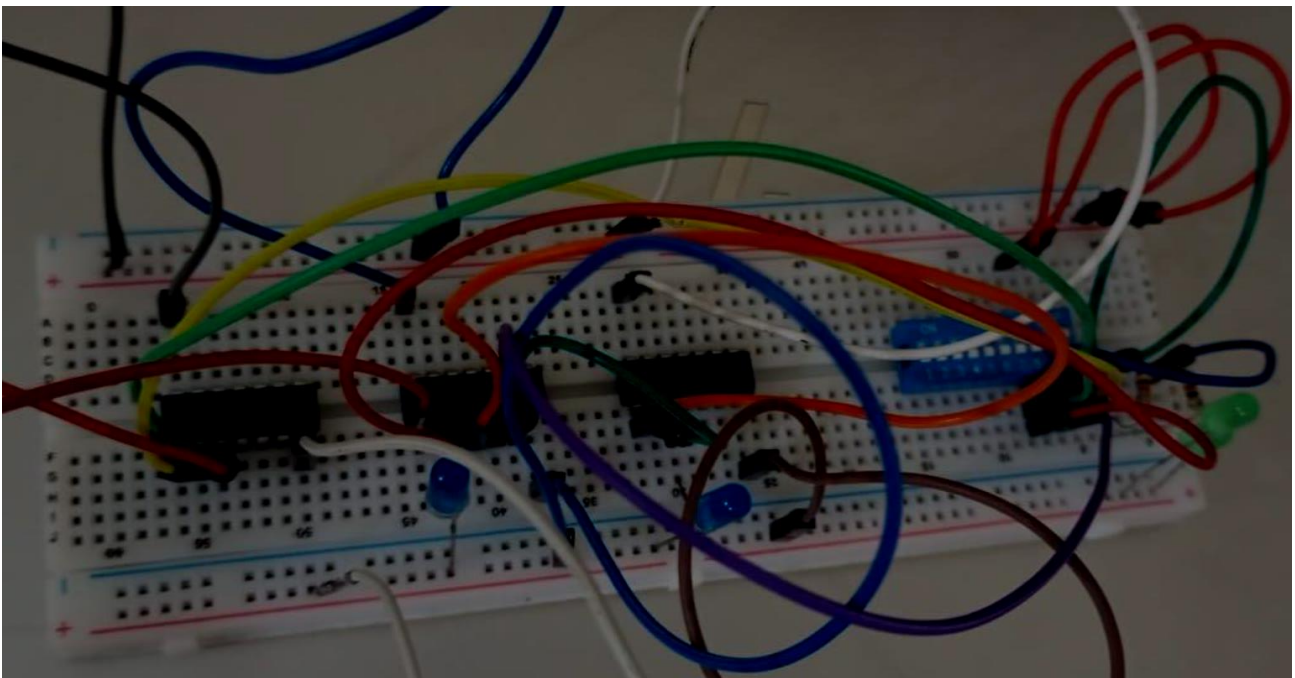Hence $\textcircled{a} = \textcircled{b}$ Proved



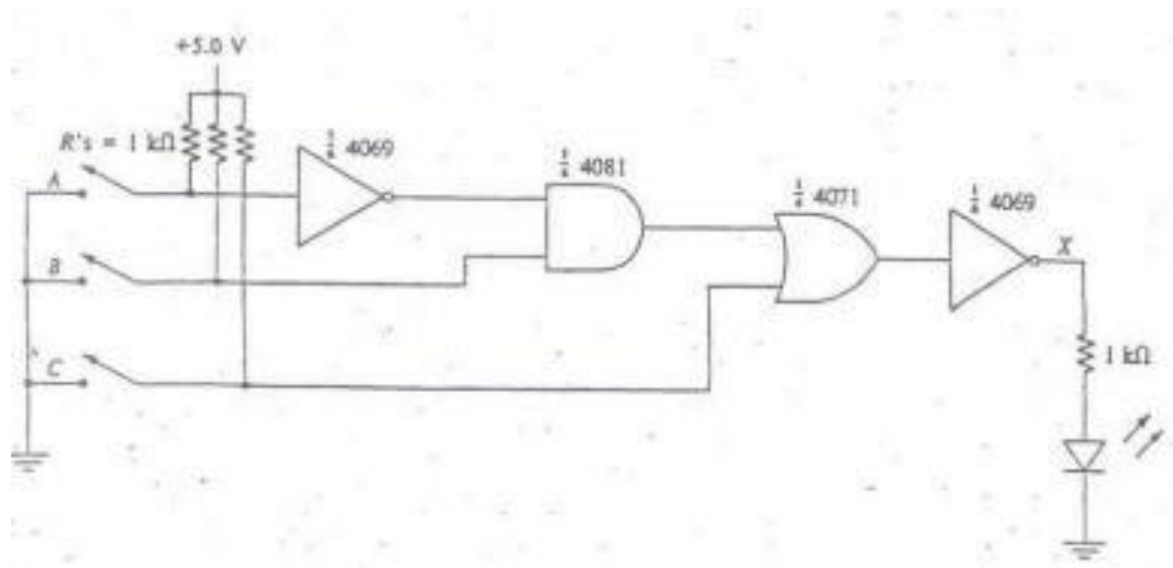

Experimental Diagram:

